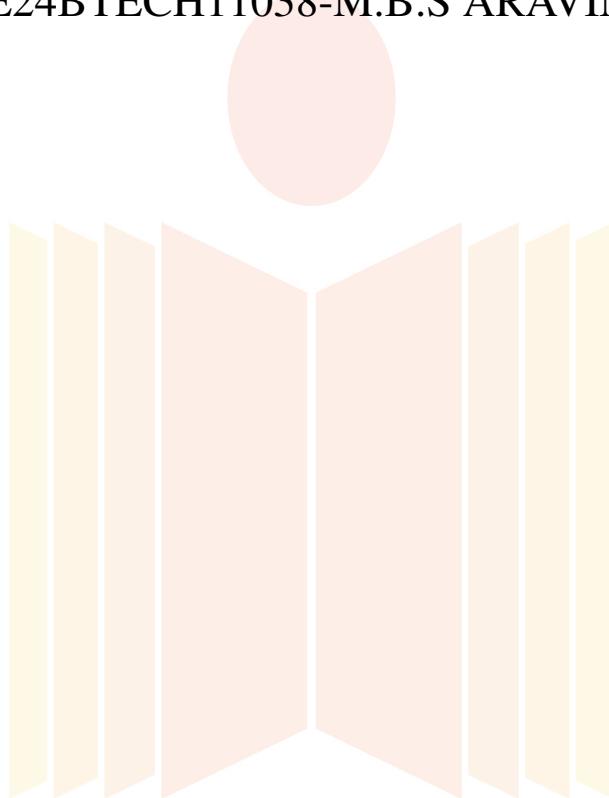


# **EE LAB REPORT-6**

**Authors:**

EE24BTECH11033-KOLLURU SURAJ

EE24BTECH11038-M.B.S ARAVIND



भारतीय प्रौद्योगिकी संस्थान हैदराबाद  
Indian Institute of Technology Hyderabad

## CONTENTS

<b>I</b>	<b>Introduction</b>	<b>3</b>
I-A	Sallen-Key:	3
I-B	Quality Factor ( $Q$ ) in Sallen-Key Second-Order Filters	3
I-C	Effect of $Q$ on Filter Response	4
I-D	Butterworth Response ( $Q \approx 0.707$ )	4
I-E	Bessel Response ( $Q \approx 0.577$ )	4
I-F	Chebyshev Response ( $Q > 0.707$ )	4
I-G	High $Q$ ( $Q > 1$ , underdamped)	4
I-H	Low $Q$ ( $Q < 0.5$ , overdamped)	4
I-I	Cutoff Frequency Formula	4
I-J	Conclusion	5
<b>II</b>	<b>Sallen-Key Low-Pass Filter (LPF)</b>	<b>6</b>
II-A	Circuit Diagram	6
II-B	Derivation of Transfer Function	6
II-C	Results	8
II-D	Bode plot	9
<b>III</b>	<b>Sallen-Key High-Pass Filter (HPF)</b>	<b>11</b>
III-A	Circuit Diagram	11
III-B	Derivation of Transfer Function	11
III-C	Results	12
III-D	Bode plot	14
<b>IV</b>	<b>Band-Pass Filter Using High-Pass and Low-Pass Filters</b>	<b>16</b>
IV-A	Introduction to Band-Pass Filters	16
IV-B	Concept of Band-Pass Filter Using High-Pass and Low-Pass Filters	16
IV-C	Circuit Diagram	16
IV-D	Transfer Function of a Band-Pass Filter	16
IV-E	Results	18
IV-F	Bode plot	20

# Sallen-Key Second-Order Low-Pass and High-Pass Filters

## I. INTRODUCTION

An Operational Amplifier (Op-Amp(LM358)) is a high-gain electronic voltage amplifier with differential inputs and a single-ended output. It is widely used in analog circuits for signal amplification, filtering, mathematical operations, and waveform shaping. By configuring external components like resistors and capacitors, op-amps can perform functions such as integration, differentiation, and summation.

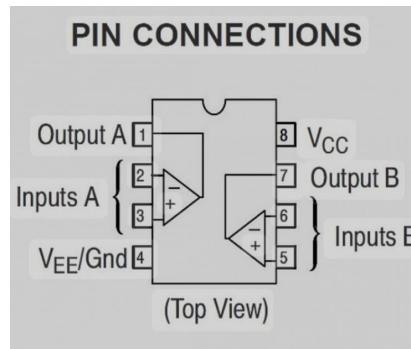


Fig. 1: LM358 connections

The LM358 is a low-power, dual operational amplifier (op-amp) designed for general-purpose applications. It operates with a wide voltage range (3V to 32V) and has low power consumption, making it ideal for battery-powered circuits. The LM358 consists of two independent op-amps in a single package, providing high gain and internal frequency compensation. It is commonly used in signal conditioning, filtering, and amplification circuits.

### A. Sallen-Key:

The Sallen-Key topology is a popular active filter design that allows the implementation of second-order low-pass and high-pass filters using operational amplifiers (op-amps), resistors, and capacitors. These filters are widely used in signal processing applications to either pass or attenuate specific frequency ranges.

### B. Quality Factor ( $Q$ ) in Sallen-Key Second-Order Filters

The **quality factor** ( $Q$ ) is a key parameter in second-order **Sallen-Key filters** (both low-pass and high-pass) that determines the selectivity and damping of the filter response. It is given by:

$$Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{(R_1 + R_2) C_2}$$

where:

- $R_1, R_2$  are the resistances in the circuit,
- $C_1, C_2$  are the capacitances,
- $Q$  influences the filter's damping and peak response.

This formula applies **identically** to both **low-pass (LPF)** and **high-pass (HPF)** Sallen-Key filters because the overall circuit topology remains the same, with only resistors and capacitors swapping positions.

### *C. Effect of $Q$ on Filter Response*

The value of  $Q$  determines the nature of the filter's frequency response:

#### *D. Butterworth Response ( $Q \approx 0.707$ )*

- **Maximally flat** response in the passband.
- No ripples, smooth transition to the stopband.
- Standard choice for general filtering applications.

#### *E. Bessel Response ( $Q \approx 0.577$ )*

- **Linear phase response**, preserving the waveform shape.
- Slower roll-off compared to Butterworth.
- Used in audio and pulse signal processing.

#### *F. Chebyshev Response ( $Q > 0.707$ )*

- **Sharper cutoff** but introduces ripples in the passband.
- Higher selectivity but at the cost of increased ringing.
- Used when a steeper roll-off is needed, like in communication systems.

#### *G. High $Q$ ( $Q > 1$ , underdamped)*

- Leads to **resonance or peaking** near the cutoff frequency.
- In extreme cases, it can cause instability or oscillations.

#### *H. Low $Q$ ( $Q < 0.5$ , overdamped)*

- Results in a **slow, gradual roll-off** with no peaking.
- Less selective filtering, useful in some smoothing applications.

#### *I. Cutoff Frequency Formula*

The **cutoff frequency** ( $f_c$ ) for a Sallen-Key second-order filter is given by:

$$f_c = \frac{1}{2\pi\sqrt{R_1R_2C_1C_2}}$$

### J. Conclusion

- Choosing  $Q$  depends on the application—**Butterworth** is ideal for general filtering, **Bessel** for phase accuracy, and **Chebyshev** for aggressive filtering.
- The **cutoff frequency** is calculated separately using  $f_c$ , which determines the transition between the passband and stopband.

This provides insight into designing Sallen-Key filters with precise frequency and damping characteristics. We will be using  $V_{CC}$  as 12V and -12V for this experiment



Fig. 2:  $V_{CC}$

भारतीय प्रौद्योगिकी संस्थान हैदराबाद  
Indian Institute of Technology Hyderabad

## II. SALLEN-KEY LOW-PASS FILTER (LPF)

A low-pass filter allows low-frequency signals to pass while attenuating high-frequency signals. The Sallen-Key second-order low-pass filter is designed using two resistors ( $R_1, R_2$ ) and two capacitors ( $C_1, C_2$ ) connected in a feedback loop with an operational amplifier.

### A. Circuit Diagram


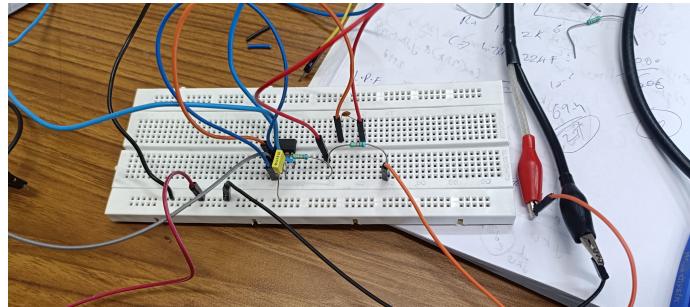


Fig. 3: Circuit for LPF Sallen-key

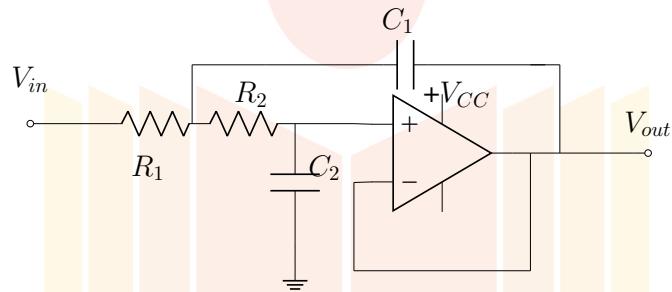

### B. Derivation of Transfer Function

Using Kirchhoff's Current Law (KCL) at the intermediate node:

$$\frac{V_{in} - V_x}{R_1} = C_1 \frac{dV_x}{dt} + \frac{V_x - V_{out}}{R_2} \quad (1)$$

where  $V_x$  is the voltage at the junction of  $R_1, R_2$ , and  $C_1$ .

Applying KCL at the output node:

$$C_2 \frac{dV_{out}}{dt} = \frac{V_x - V_{out}}{R_2} \quad (2)$$

Taking the Laplace transform:

$$\frac{V_{in} - V_x}{R_1} = sC_1 V_x + \frac{V_x - V_{out}}{R_2} \quad (3)$$

$$sC_2 V_{out} = \frac{V_x - V_{out}}{R_2} \quad (4)$$

Solving these equations step by step:

Express  $V_x$  in terms of  $V_{in}$  and  $V_{out}$ .

Substitute into the second equation.

Solve for  $H(s) = \frac{V_{\text{out}}}{V_{\text{in}}}$ .

After simplification, the transfer function is:

$$H(s) = \frac{A}{s^2 + \frac{\omega_c}{Q}s + \omega_c^2} \quad (5)$$

where:

$$\omega_c = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \quad (6)$$

$$Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{(R_1 + R_2) C_2} \quad (7)$$

Where  $C_2$  is the capacitor whose one end is connected to ground.

For a unity-gain Sallen-Key low-pass filter,  $A = 1$ .

We have a unity-gain Sallen-Key low-pass filter so our transfer function equation is

$$H(s) = \frac{1}{s^2 + \frac{\omega_c}{Q}s + \omega_c^2} \quad (8)$$

The values of R and C for this LPF are

$$R_1 = 68k\Omega$$

$$R_2 = 68k\Omega$$

$$C_1 = 10nF$$

$$C_2 = 4.7nF$$

Theoretical cutoff frequency will be

$$f_c = \frac{1}{2\pi\sqrt{R_1 R_2 R_3 R_4}}$$

$$f_c = \frac{1}{2\pi\sqrt{68 \times 10^3 \times 68 \times 10^3 \times 10 \times 10^{-9} \times 4.7 \times 10^{-9}}}$$

**भारतीय प्रौद्योगिकी संसाधन हैदराबाद**

At cutoff frequency we should be getting magnitude of -3Db  
*Calculation of Quality factor::*

$$\sqrt{68k \times 68k \times 10n \times 4.7n} = \sqrt{2.176} \approx 1.475$$

$$(68k + 68k) \times 4.7n = 136k \times 4.7n = 639.2 \times 10^{-6}$$

$$Q = \frac{1.475}{639.2 \times 10^{-6}} \approx 0.72$$

*Final Answer::*

$$Q \approx 0.72$$

It is nearer to 0.77 so we will get clean bode plot

### C. Results

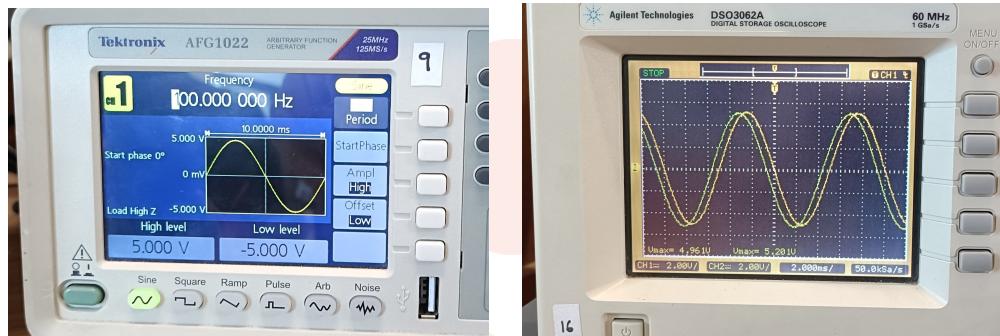


Fig. 4

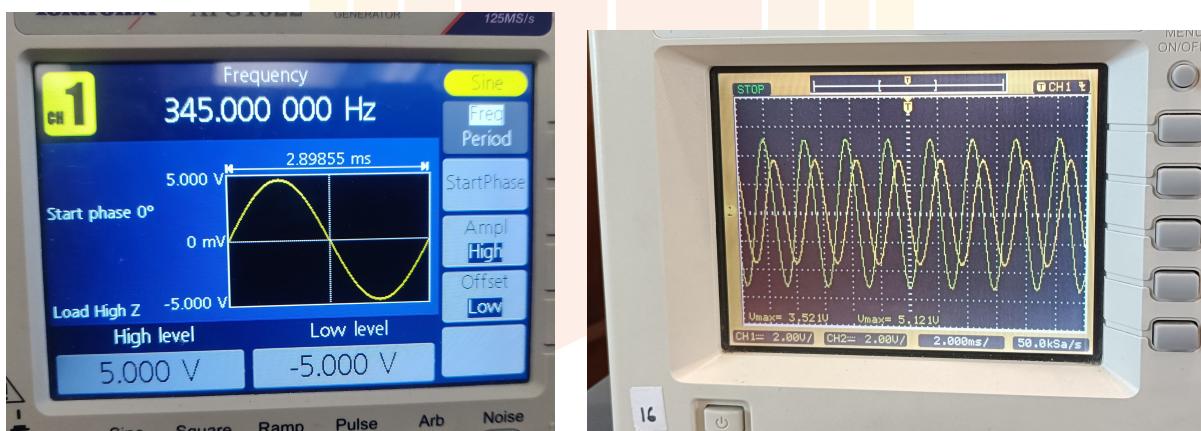


Fig. 5

भारतीय प्रौद्योगिकी संस्थान हैदराबाद

Indian Institute of Technology Hyderabad



Fig. 6

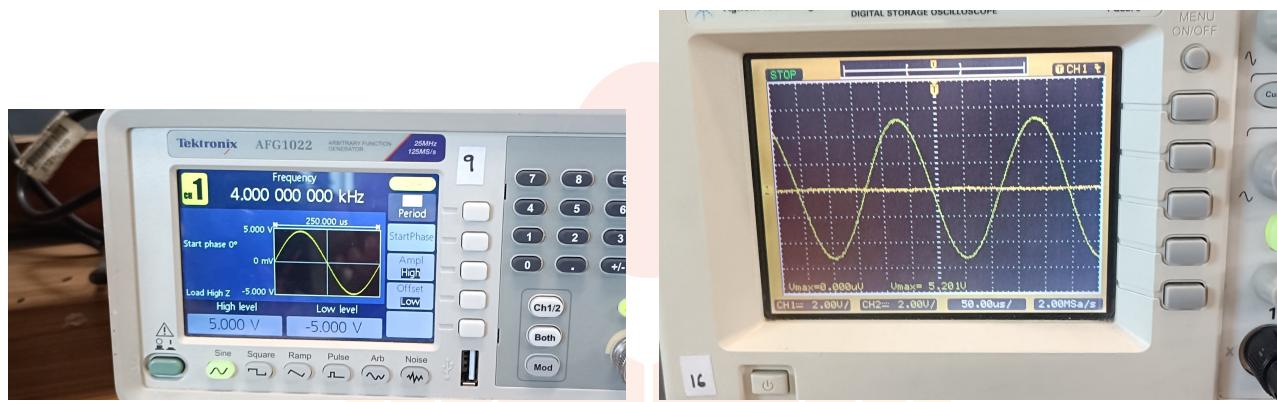


Fig. 7

Frequency (Hz)	Magnitude (dB)
0.1	-0.07
345	-3.05
1000	-19.02
4000	-33.98

TABLE I: Results of LPF  
भारतीय प्रौद्योगिका संस्थान हैदराबाद

#### D. Bode plot

Indian Institute of Technology Hyderabad

Bode plots are plotted using Results obtained

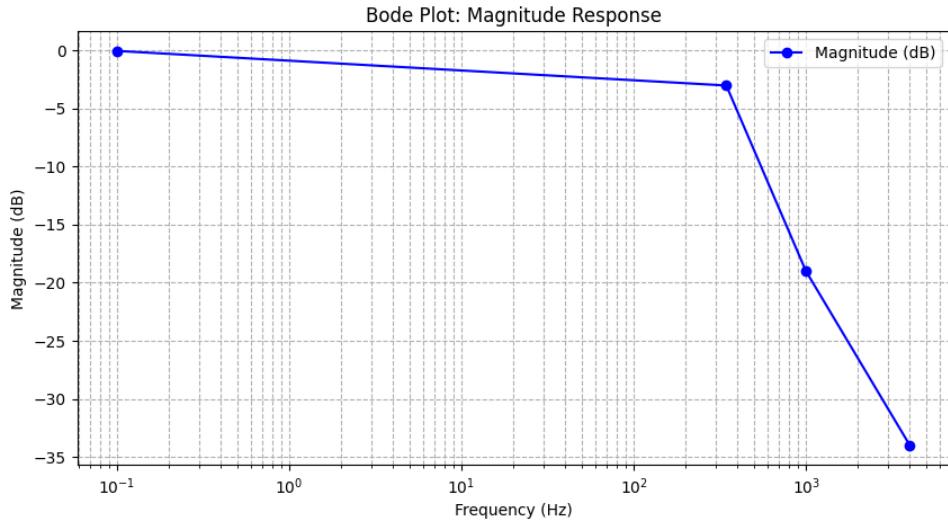


Fig. 9: Python generated plot from values obtained

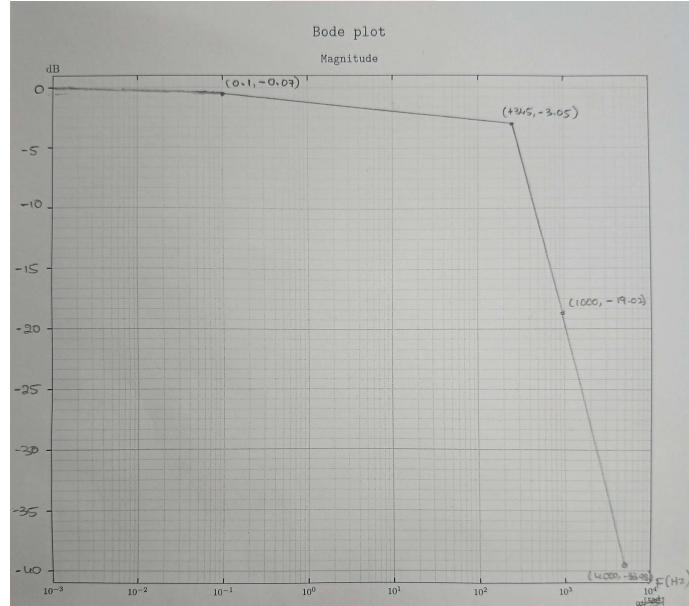


Fig. 8: Hand-plotted LPF bode plot(magnitude vs frequency)

भारतीय प्रौद्योगिकी संस्थान हैदराबाद  
Indian Institute of Technology Hyderabad

### III. SALLEN-KEY HIGH-PASS FILTER (HPF)

A high-pass filter allows high-frequency signals to pass while attenuating low-frequency signals. The Sallen-Key second-order high-pass filter uses a similar topology but with capacitors and resistors swapped in position.

#### A. Circuit Diagram

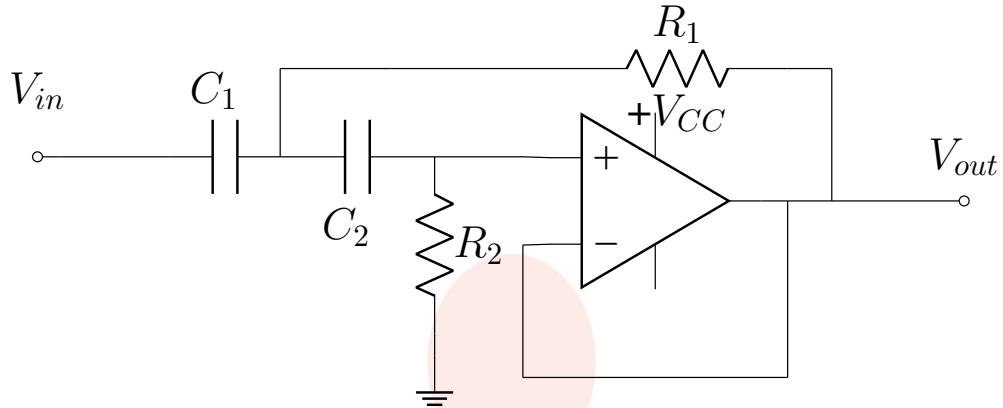


Fig. 10: Circuit Diagram for sallen-key HPF

#### B. Derivation of Transfer Function

Using KCL at the intermediate node:

$$C_1 \frac{dV_{in}}{dt} = \frac{V_x}{R_1} + C_1 \frac{dV_x}{dt} \quad (9)$$

Applying KCL at the output node:

$$\frac{V_x}{R_2} + C_2 \frac{dV_{out}}{dt} = 0 \quad (10)$$

Taking the Laplace transform:

$$sC_1 V_{in} = \frac{V_x}{R_1} + sC_1 V_x \quad (11)$$

$$\frac{V_x}{R_2} + sC_2 V_{out} = 0 \quad (12)$$

Solving these equations step by step, the transfer function is:

$$H(s) = \frac{As^2}{s^2 + \frac{\omega_c}{Q}s + \omega_c^2} \quad (13)$$

where  $\omega_c$  and  $Q$  are defined as in the low-pass filter case.

$$\omega_c = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \quad (14)$$

$$Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{(R_1 + R_2) C_2} \quad (15)$$

For a unity-gain Sallen-Key low-pass filter,  $A = 1$ .

We have a unity-gain Sallen-Key low-pass filter so our transfer function equation is

$$H(s) = \frac{1}{s^2 + \frac{\omega_c}{Q}s + \omega_c^2} \quad (16)$$

The values of R and C for this HPF are

$$R_1 = 68k\Omega$$

$$R_2 = 68k\Omega$$

$$C_1 = 10\mu F$$

$$C_2 = 1\mu F$$

The critical frequency  $f_c$  is given by:

$$f_c = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$$

Substituting the values:

$$f_c = \frac{1}{2\pi\sqrt{(68 \times 10^3)(68 \times 10^3)(10 \times 10^{-6})(1 \times 10^{-6})}}$$

$$f_c = \frac{1}{2\pi \times 0.000215}$$

$$f_c \approx 0.740 \text{ Hz}$$

### C. Results



Fig. 11

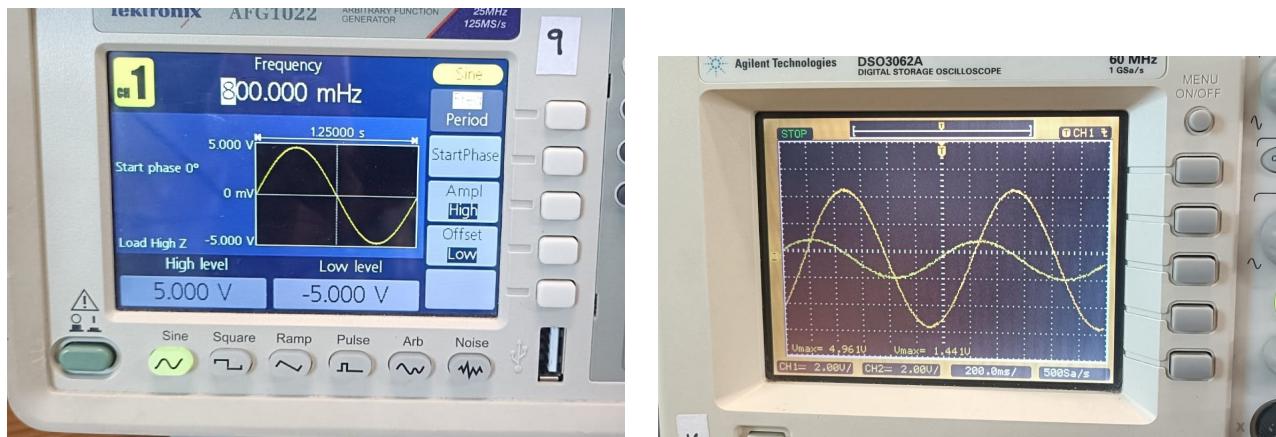


Fig. 12


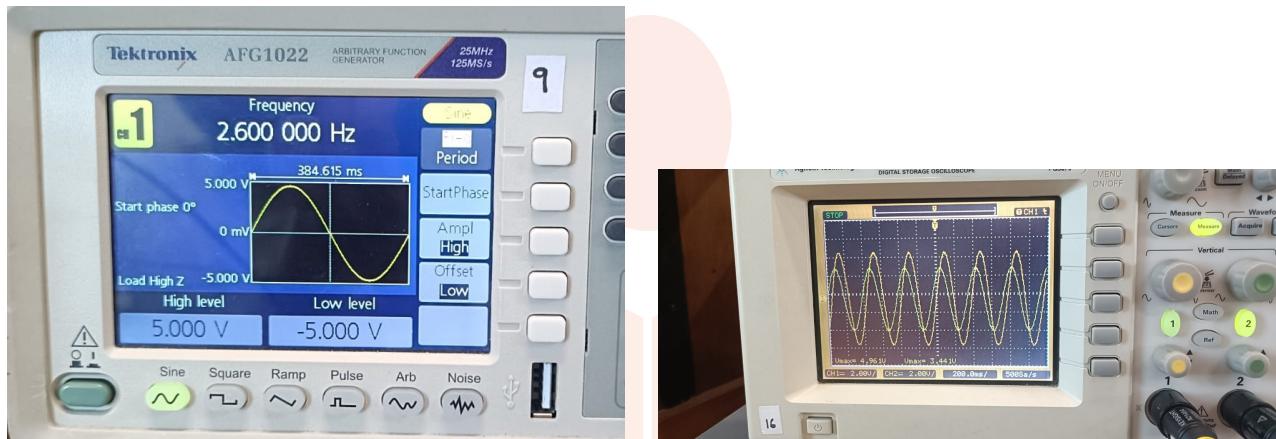


Fig. 13

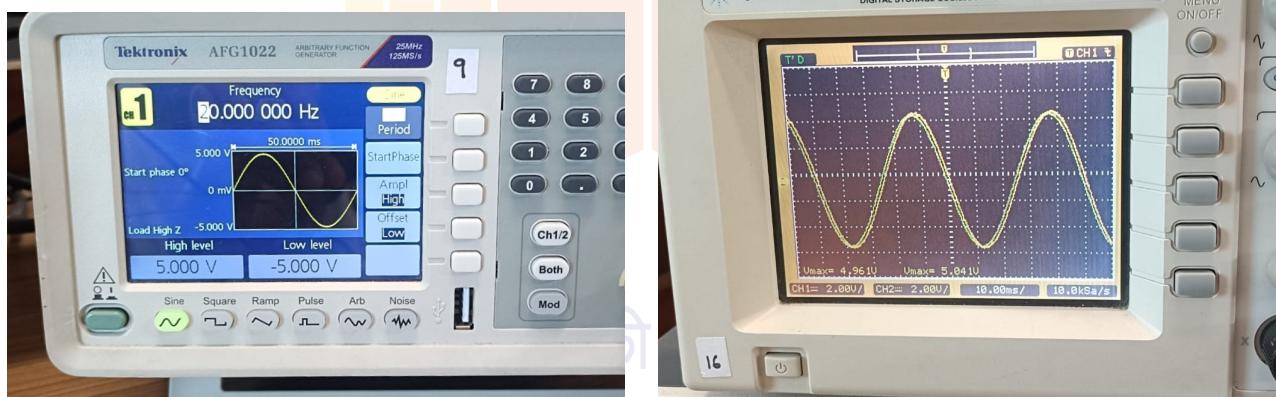

Indian Institute of Technology Hyderabad



Fig. 15

Frequency (Hz)	Magnitude (dB)
0.1	-26.375
0.8	-10.81
2.6	-3.24
20	-0.07
100	-0.02

TABLE II: Results of HPF

#### D. Bode plot

Bode plots are plotted using Results obtained

भारतीय प्रौद्योगिकी संस्थान हैदराबाद  
Indian Institute of Technology Hyderabad

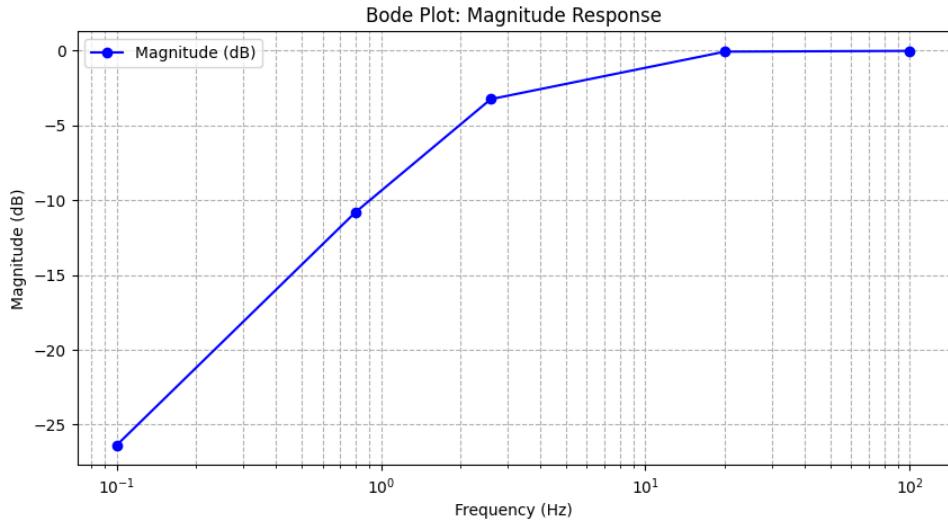


Fig. 17: Python generated plot from values obtained

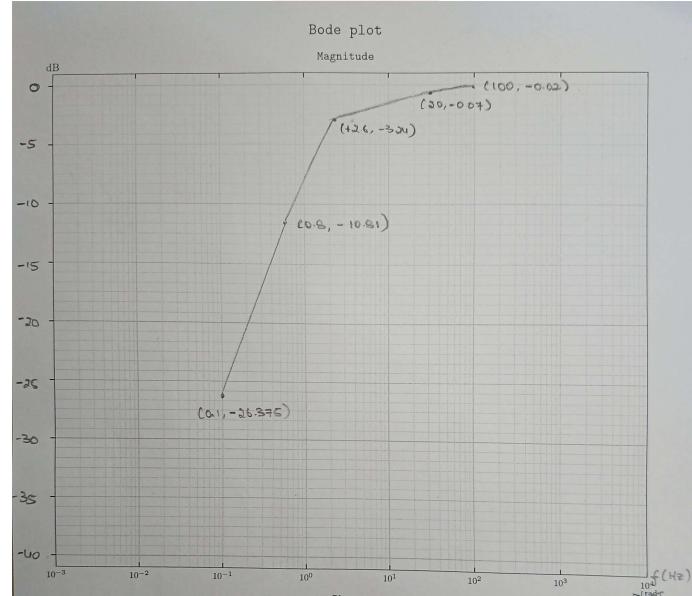


Fig. 16: Hand-plotted HPF bode plot(magnitude vs frequency)

भारतीय प्रौद्योगिकी संस्थान हैदराबाद  
Indian Institute of Technology Hyderabad

## IV. BAND-PASS FILTER USING HIGH-PASS AND LOW-PASS FILTERS

### A. Introduction to Band-Pass Filters

A **Band-Pass Filter (BPF)** is an electronic circuit that allows frequencies within a specific range to pass while attenuating frequencies outside this range. It is essentially a combination of a **low-pass filter (LPF)** and a **high-pass filter (HPF)**, where the LPF eliminates high-frequency components, and the HPF removes low-frequency components, allowing only the desired frequency range to pass through. Band-pass filters are widely used in communication systems, audio processing, signal processing, and various electronic applications.

### B. Concept of Band-Pass Filter Using High-Pass and Low-Pass Filters


A **band-pass filter (BPF)** can be constructed by cascading a high-pass filter and a low-pass filter in series. The high-pass filter removes low-frequency components, while the low-pass filter suppresses high-frequency components. As a result, only frequencies between the cutoff frequencies  $\omega_L$  and  $\omega_H$  are passed, forming a band of frequencies.

**The output of the HPF should be connected to the input of the LPF to achieve the desired band-pass response.**

In this configuration:

- The **low-pass filter (LPF)** consists of resistors  $R_3, R_4$  and capacitors  $C_3, C_4$ .
- The **high-pass filter (HPF)** consists of resistors  $R_1, R_2$  and capacitors  $C_1, C_2$ .

### C. Circuit Diagram

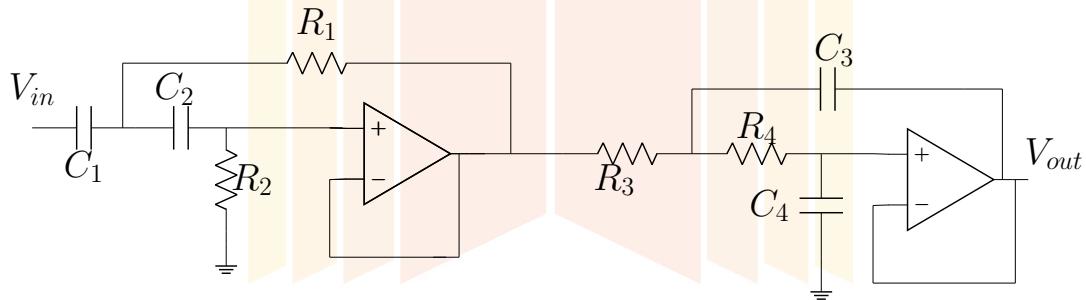

### D. Transfer Function of a Band-Pass Filter

The transfer function of a second-order **Sallen-Key Band-Pass Filter** formed using a separate HPF and LPF is given by:

$$H(s) = H_{LPF}(s) \cdot H_{HPF}(s) \quad (17)$$

where:

$$H_{LPF}(s) = \frac{1}{1 + s \left( \frac{R_3+R_4}{R_3R_4C_4} \right) + s^2 \left( \frac{1}{R_3R_4C_3C_4} \right)} \quad (18)$$

$$H_{HPF}(s) = \frac{s^2}{s^2 + s \left( \frac{R_1+R_2}{R_1R_2C_2} \right) + \frac{1}{R_1R_2C_1C_2}} \quad (19)$$

Center Frequency and Quality Factor:

The **center frequency**  $\omega_C$  (resonant frequency) of the band-pass filter is given by:

$$\boxed{\omega_C = \sqrt{\omega_L \cdot \omega_H}} \quad (20)$$

At the resonance frequency  $f_C$ , the output gain is maximum, and the phase shift is typically  $0^\circ$  (for Butterworth filters). The circuit exhibits maximum energy exchange between reactive components, with the quality factor  $Q$  determining the bandwidth, where higher  $Q$  leads to a narrower passband. The group delay is minimal or stable near  $f_C$ , ensuring minimal signal distortion.

where  $\omega_L$  and  $\omega_H$  are the cutoff frequencies of the HPF and LPF, respectively.

### Characteristics of Band-Pass Filters:

- **Frequency Selection:** Band-pass filters allow frequencies within a certain range to pass while attenuating both low and high frequencies outside the passband.
- **Center Frequency ( $f_0$ ):** The frequency at which the gain is maximum.
- **Bandwidth (BW):** The range of frequencies between the lower cutoff frequency  $f_L$  and the upper cutoff frequency  $f_H$ , given by:

$$BW = f_H - f_L \quad (21)$$

- **Quality Factor (Q):** The measure of how selective the filter is, given by:

$$Q = \frac{f_C}{f_H - f_L} \quad (22)$$

- A higher  $Q$  results in a **narrow** band-pass filter, allowing only a small range of frequencies.
- A lower  $Q$  value results in a **wider bandwidth**.

## E. Results

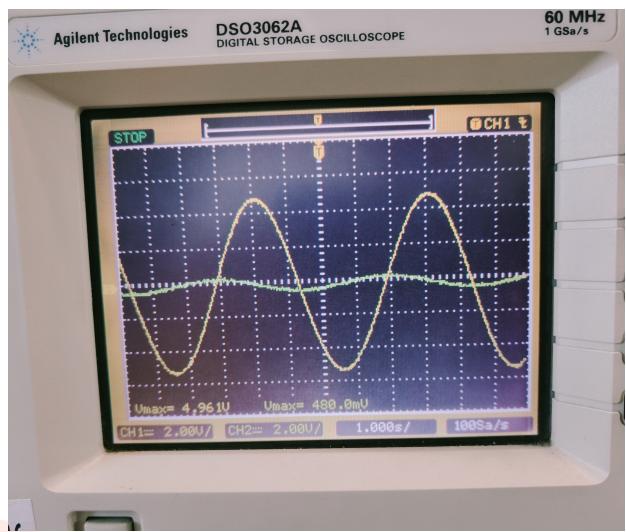


Fig. 18

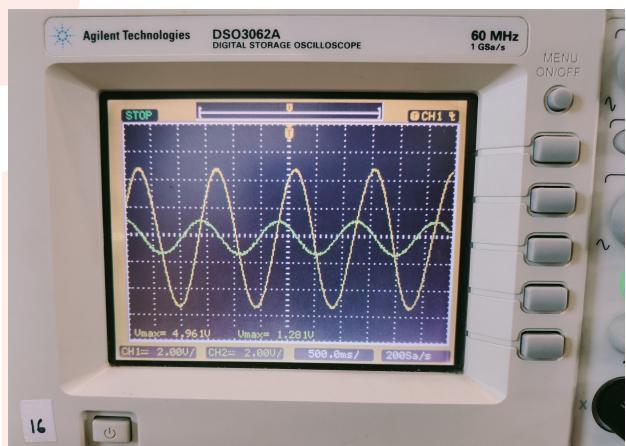
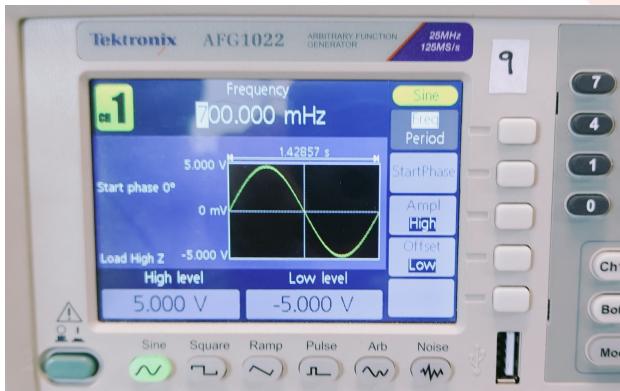


Fig. 19

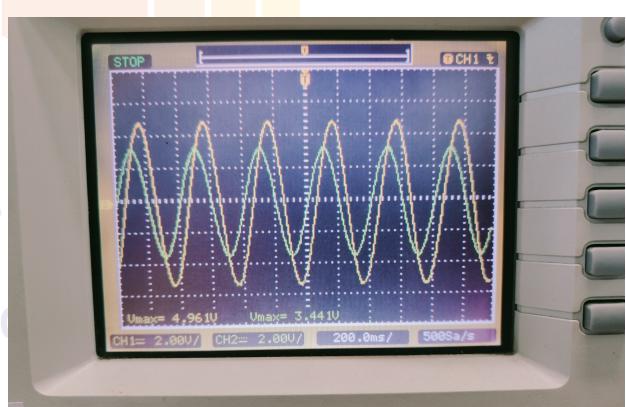
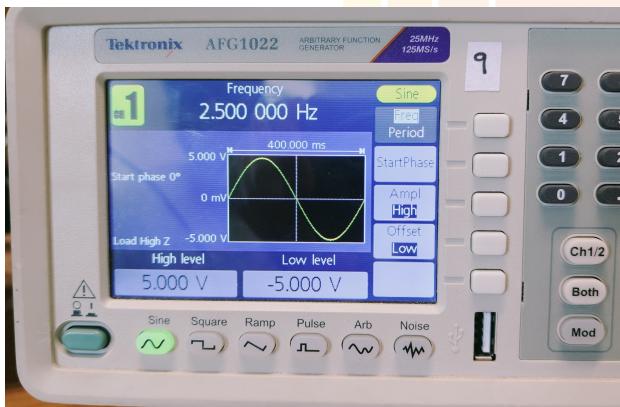


Fig. 20

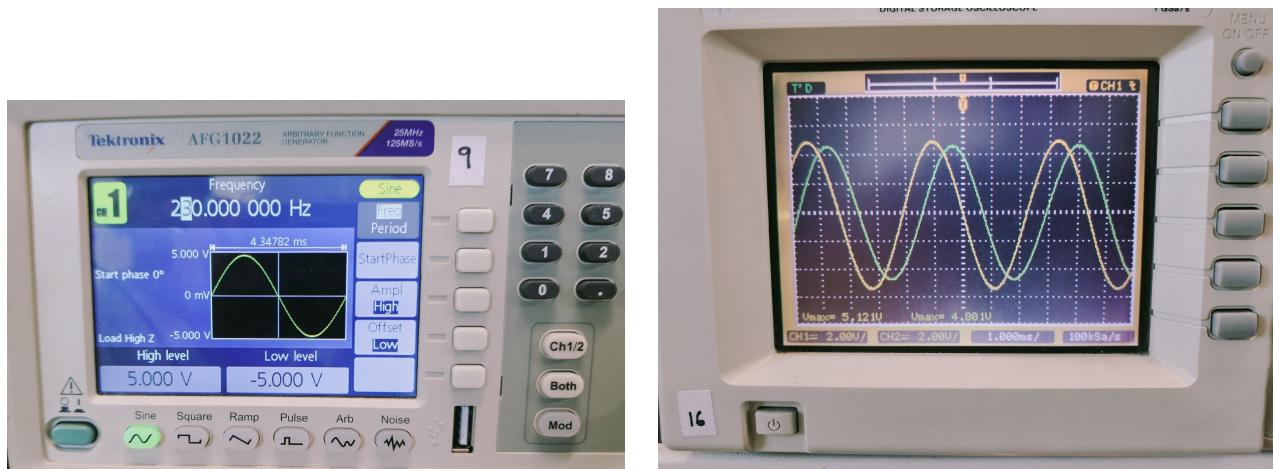


Fig. 21

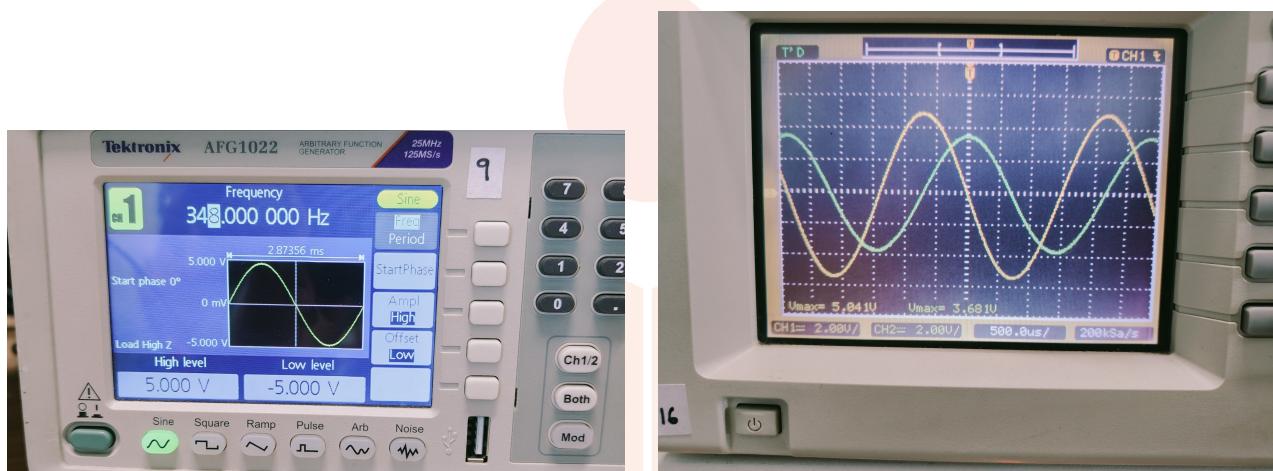


Fig. 22

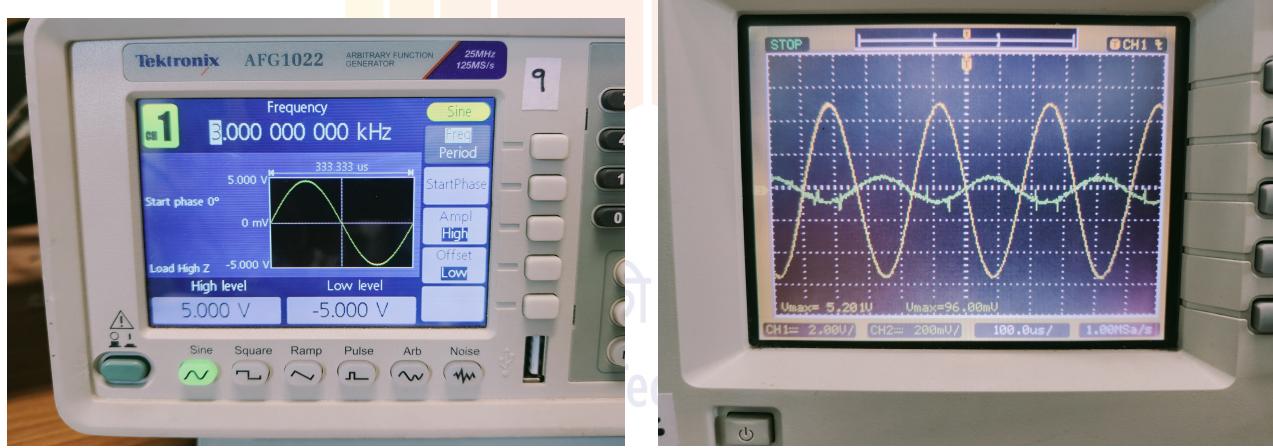


Fig. 23

Here is case where output is maximum i.e resonant frequency

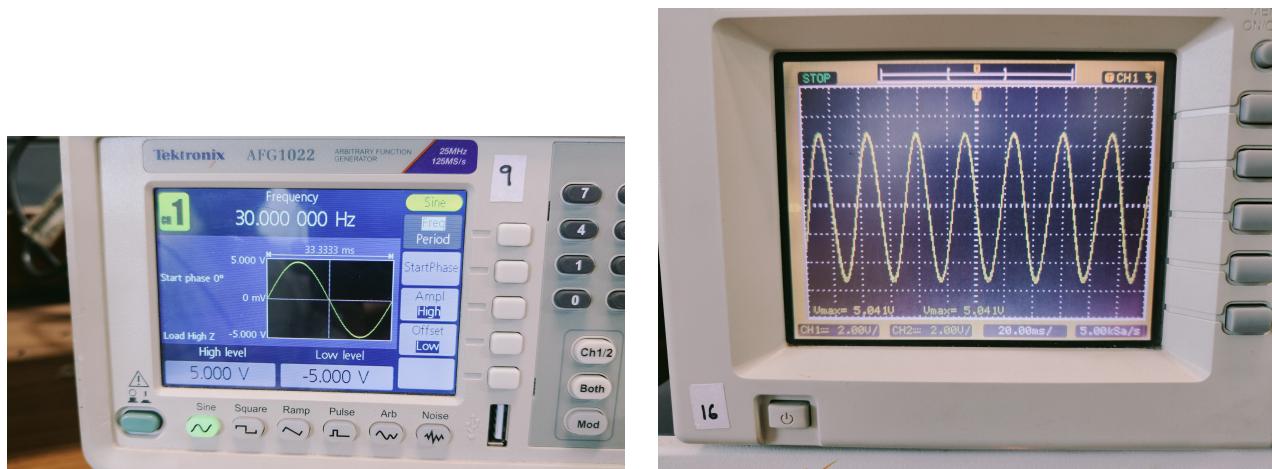


Fig. 24

Frequency (Hz)	Magnitude (dB)
0.2	-20.35
2.5	-3.24
30	0.00
230	-0.53
1000	-15.09
3000	-34.33

TABLE III: Results of Bandpass filter

#### F. Bode plot

Bode plots are plotted using Results obtained

भारतीय प्रौद्योगिकी संस्थान हैदराबाद  
Indian Institute of Technology Hyderabad

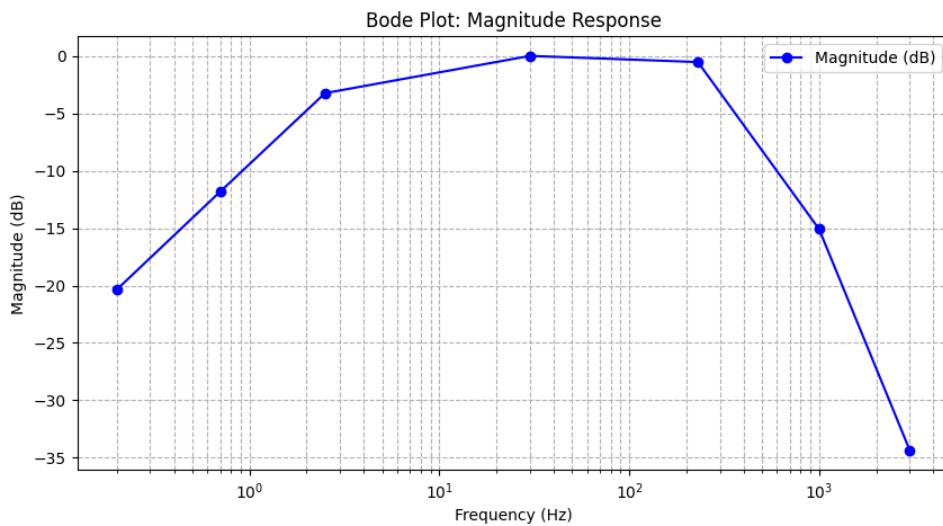


Fig. 26: Python generated plot from values obtained

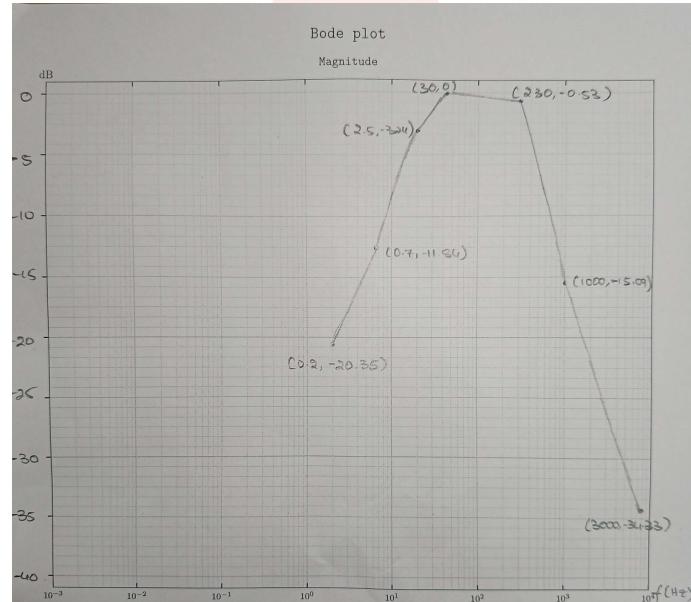


Fig. 25: Hand-plotted BPF bode plot(magnitude vs frequency)

भारतीय प्रौद्योगिकी संस्थान हैदराबाद  
Indian Institute of Technology Hyderabad