

# EE LAB REPORT-3

**Kolluru Suraj**  
**EE24BTECH11033**  
**Department of EE**

**M.B.S Aravind**  
**EE24BTECH11038**  
**Department of EE**

## CONTENTS

-A	Aim . . . . .	2
-B	Appratus used . . . . .	2
-C	Theory . . . . .	2
-D	Procedure/Experiment . . . . .	3
<b>I</b>	<b><u>Stage -1</u></b>	<b>4</b>
<b>II</b>	<b><u>Stage -2</u></b>	<b>8</b>
<b>III</b>	<b><u>Stage -3</u></b>	<b>11</b>

### A. Aim

This experiment focuses on obtaining Bode plots (magnitude and phase response) for 1-stage, 2-stage, and 3-stage RC low-pass filters using an oscilloscope and function generator. RC low-pass filters attenuate high-frequency signals while allowing low-frequency signals to pass, with their cutoff frequency determined by the resistor (R) and capacitor (C) values.

### B. Apparatus used

- Cathode Ray Oscilloscope (CRO).
- Breadboard.
- Function Generator
- BNC Cables.
- Connecting wires.
- Capacitor( $100\mu F$ )
- Resistor( $2K\Omega$ )

In our experiment, the value of RC is **0.2 sec**

### C. Theory

#### Transfer function

- 1) The transfer function of a circuit is the ratio of the output signal (voltage or current) to the input signal (voltage or current) in the frequency domain (s-domain). It describes how the circuit responds to different frequencies.

$$H(s) = \frac{V_{out}}{V_{in}} \text{ or } \frac{I_{out}}{I_{in}} \text{ (where } s = j\omega) \quad (1)$$

- 2) From  $H(s)$  we can calculate gain(in dB) defined as

$$\text{Gain} = 20\log_{10}(H(s))$$

- 3) From the transfer function, we can also calculate the phase difference which is given by

$$\text{phase}(\omega) = \arg(H(s)) \quad (2)$$

- 4) The transfer function helps determine the frequency response of a circuit, showing how the circuit amplifies or attenuates different frequencies. This is particularly useful in filters (e.g., low-pass, high-pass, band-pass).

## Bode plots

- 1) A Bode plot is a graphical representation of a system's frequency response. It consists of two separate plots:
  - Magnitude plot (Gain vs log(Frequency))
  - Phase plot (phase vs log(Frequency))

### Magnitude plot

- X-axis : Logarithmic scale of frequency.
- Y-axis :  $20\log_{10}(H(s))$  (Magnitude in dB)

### Phase plot

- X-axis : Logarithmic scale of frequency.
- Y-axis :  $\angle H(jw)$

## D. Procedure/Experiment

- 1) Connect the resistors and capacitors in each stage (Stage-1, Stage-2, Stage-3) such that the output of one RC network feeds into the input of the next, maintaining a cascaded configuration for cumulative frequency response analysis
- 2) Use a function generator to apply a sine wave of amplitude 5 input across the RC circuit
- 3) Use the oscilloscope to display both the input and output waveforms
  - Connect Channel 1 across the capacitor to observe the output.
  - Connect Channel 2 to the input (sine wave).
- 4) To calculate the voltage across the capacitor follow these steps
  - a) By using the cursors measure the voltage across the capacitor and label it as  $V_{out}$
  - b) Plot the Bode magnitude response by measuring  $20\log \frac{V_{out}}{V_{in}}$  (in dB) for each stage (Stage-1, Stage-2, Stage-3) across a logarithmic frequency scale to analyze the gain roll-off of the RC circuit.
- 5) To calculate the phase difference, follow these steps
  - a) **Calculate  $\Delta X$ (horizontal shift)**
    - Display both the  $V_{out}$  and  $V_{in}$  wave forms on the oscilloscope
    - Align there Zero-crossing points horizontally
    - Use the oscilloscope's cursor tool to measure the horizontal distance ( $\Delta x$ ) between the corresponding zero crossings  $V_{in}$  and  $V_{out}$  (rising/falling edge to rising/falling edge )

Now, the phase difference is given by  $\theta = (\frac{\Delta X}{T})360^\circ$ . It gives  $\theta$  in degrees

## I. STAGE -1

The circuit will be as following

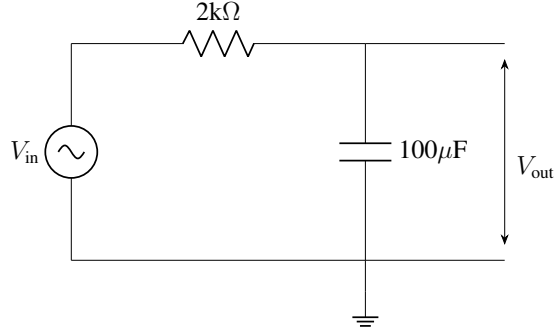


Fig. 1: Circuit Diagram

**Calculating transfer function**

$$\begin{aligned}
 \frac{V_{out}}{V_{in}} &= \frac{\text{Voltage across capacitor}}{V_{in}} \\
 &= \frac{\text{Reactance of capacitor}}{\text{impedance}} \\
 &= \frac{\frac{1}{sC}}{\frac{1}{sC} + R} \\
 H(s) &= \frac{1}{1 + sRC} \\
 H(j\omega) &= \frac{1}{1 + j\omega RC} \\
 \text{Gain} &= 20\log_{10}|H(j\omega)| \\
 &= 20\log_{10}\left(\frac{1}{\sqrt{1 + (\omega RC)^2}}\right) \\
 &= 20\log_{10}\left(\frac{1}{\sqrt{1 + (4 \times 10^{-2})(\omega)^2}}\right) \\
 \text{Phase} &= \arg(H(s)) \\
 &= -\tan^{-1}(\omega RC)
 \end{aligned}$$

1) If we cascade N identical RC filters, the overall transfer function is given by

$$\begin{aligned}
 H_N(s) &= \left( \frac{1}{1 + sRC} \right)^N \\
 \text{Gain} &= 20 \times \log_{10} |H_N(s)| \\
 &= 20 \times N \log_{10} \left( \frac{1}{\sqrt{1 + (\omega RC)^2}} \right) \\
 &= -10 \times N \log(1 + (\omega RC)^2) \\
 \text{Phase} &= -N \tan^{-1} \omega RC
 \end{aligned}$$

**If the phase crosses -180 we will add +360 to phase to make sure that it is in range of 180 to -180**

By varying the frequency and calculating the transfer function and phase, we will obtain the below table for stage -1

Here are the figures observed on Oscilloscope for different range of frequencies

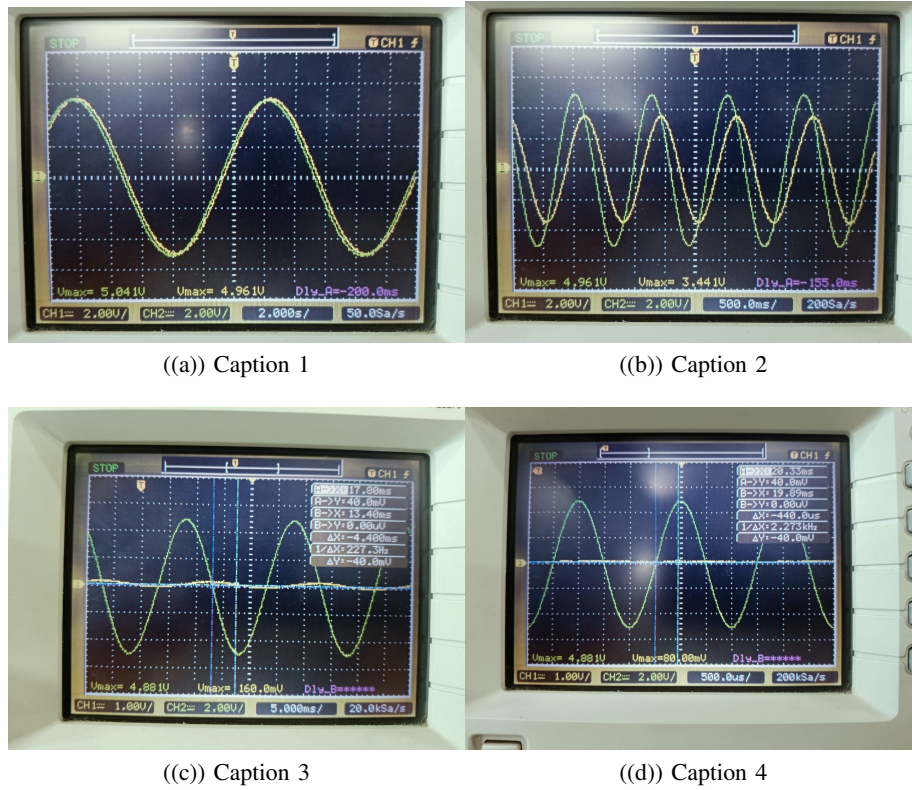


Fig. 2: Stage-1 figures

By varying the frequency and calculating the transfer function and phase, we obtained the final values from oscilloscope

Frequency	H(s)	Phase
0.08 Hz	-0.0697	-5.76
0.8 Hz	-3.0033	-44.64
50	-40.0464	-79.2
500 Hz	-60.046	-89.4

These are the bode plots obtained

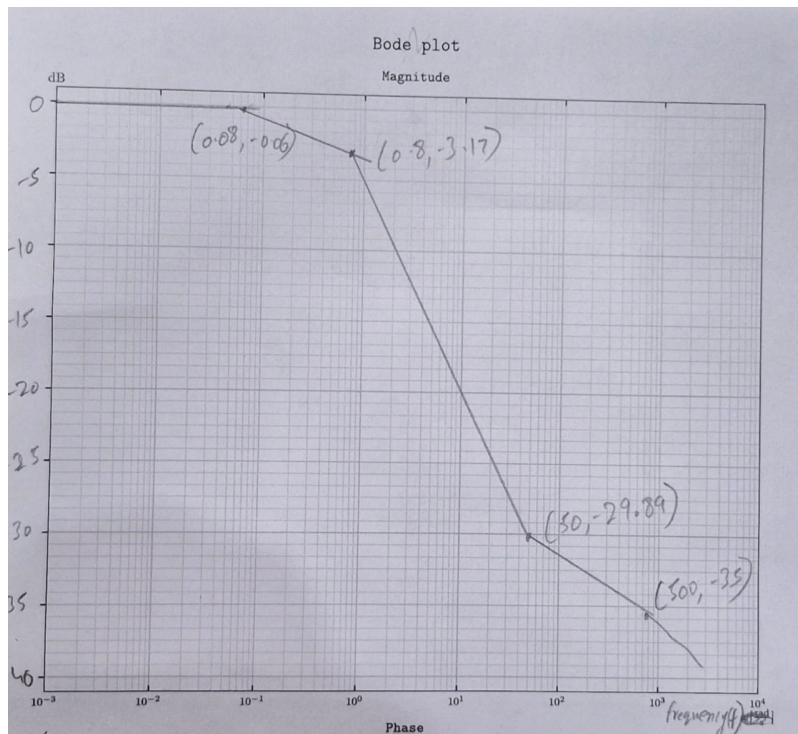


Fig. 3: stage-1 magnitude

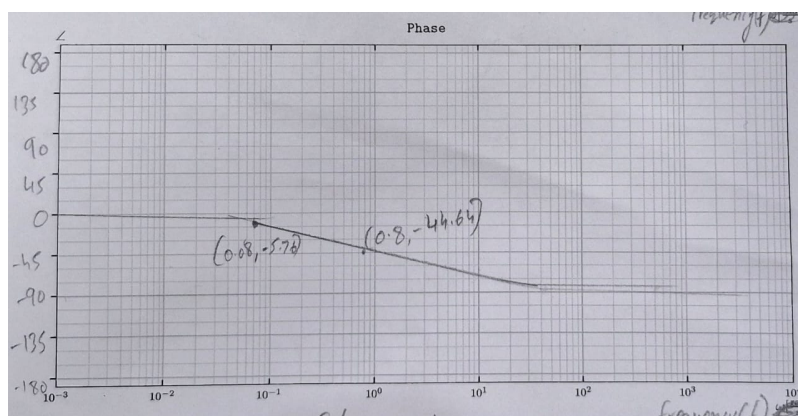


Fig. 4: Stage-1 phase

## II. STAGE -2

The circuit will be as following

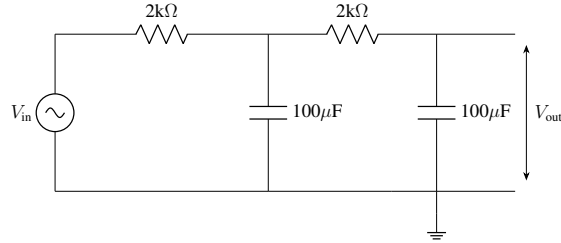


Fig. 5: RC Circuit Diagram

The transfer function for Stage -2 is

$$H_2(s) = \left( \frac{1}{1 + sRC} \right)^2$$

$$\begin{aligned} \text{Gain} &= -10 \times 2 \log(1 + (\omega RC)^2) \\ &= -20 \log(1 + (\omega RC)^2) \end{aligned}$$


$$\begin{aligned} \text{Phase} &= \arg(H(s)) \\ &= -2 \tan^{-1}(\omega RC) \end{aligned}$$

By varying the frequency and calculating the transfer function and phase, we will obtain the below table for stage -2


Frequency	H(s)	Phase
0.08 Hz	-0.354	-18.43
0.8 Hz	-9.67	-89.28
50	-55.0464	-170.2
500 Hz	-75.046	-179.2

These are the bode plots obtained




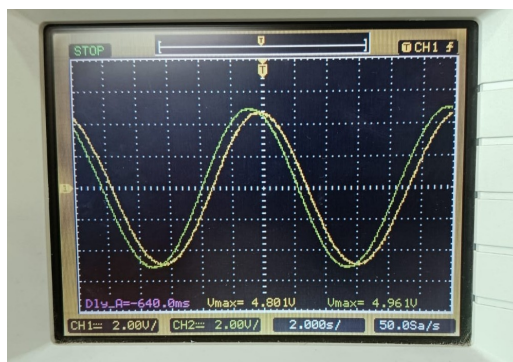


((a)) Caption 1

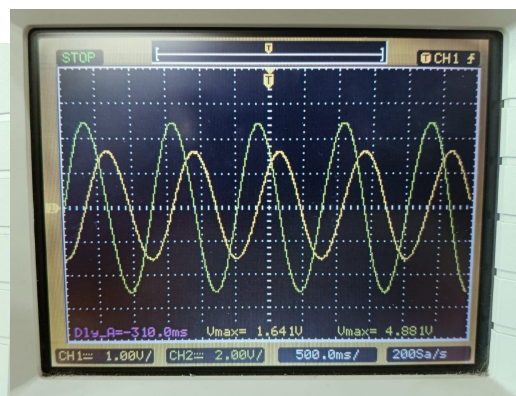

((b)) Caption 2

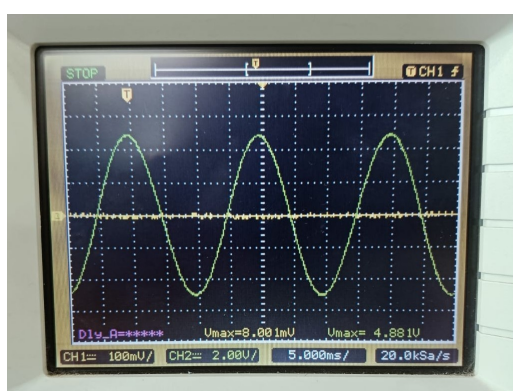


((c)) Caption 3

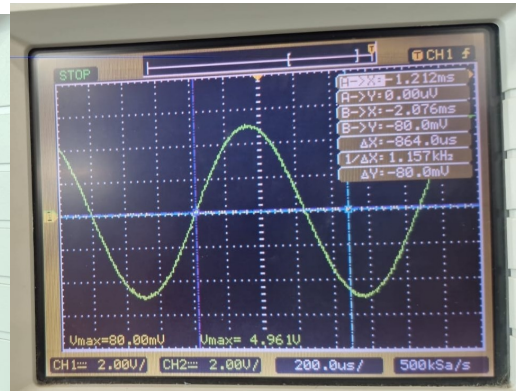

((d)) Caption 4

Fig. 6: Stage-2

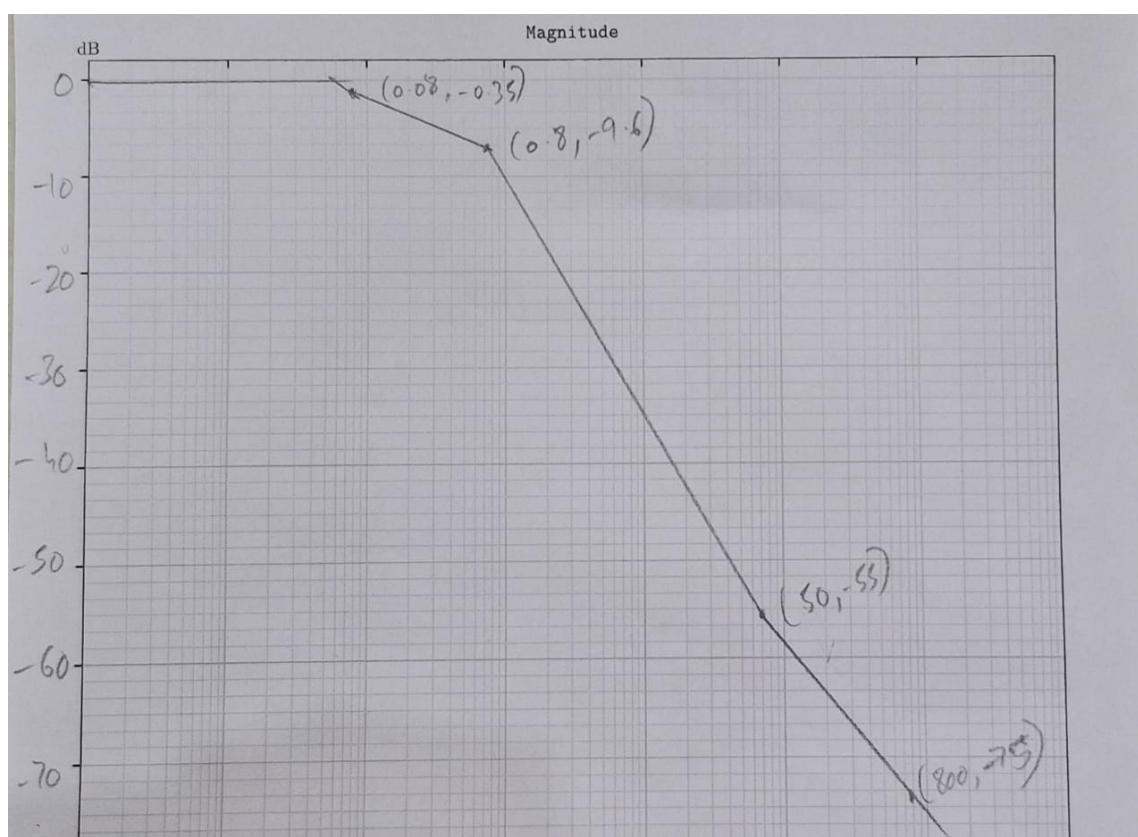

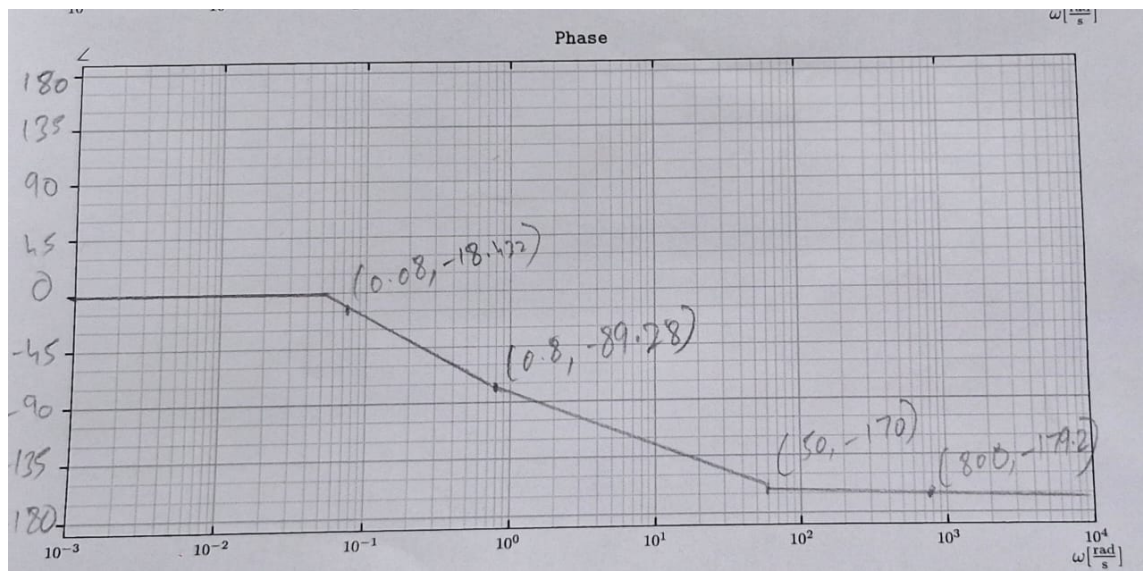


Fig. 8: stage-2 phase

### III. STAGE -3

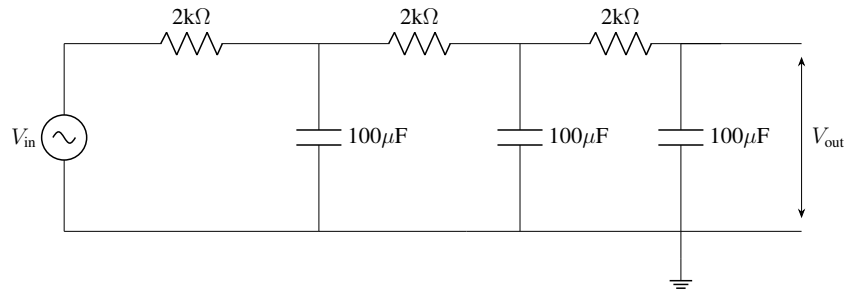


Fig. 9: Three-Stage RC Low-Pass Filter

The transfer function for Stage -3 is

$$H_3(s) = \left( \frac{1}{1 + sRC} \right)^3$$


$$\begin{aligned} \text{Gain} &= -10 \times 3 \log(1 + (\omega RC)^2) \\ &= -30 \log(1 + (\omega RC)^2) \end{aligned}$$

$$\begin{aligned} \text{Phase} &= \arg(H(s)) \\ &= -3 \tan^{-1}(\omega RC) \end{aligned}$$

By varying the frequency and calculating the transfer function and phase, we will obtain the below table for stage -3


Frequency	H(s)	Phase
0.08 Hz	-0.554	-27.43
0.8 Hz	-12.38	-132.28
80	-55.0464	168.2
800 Hz	-75.046	111.2

These are the bode plots obtained

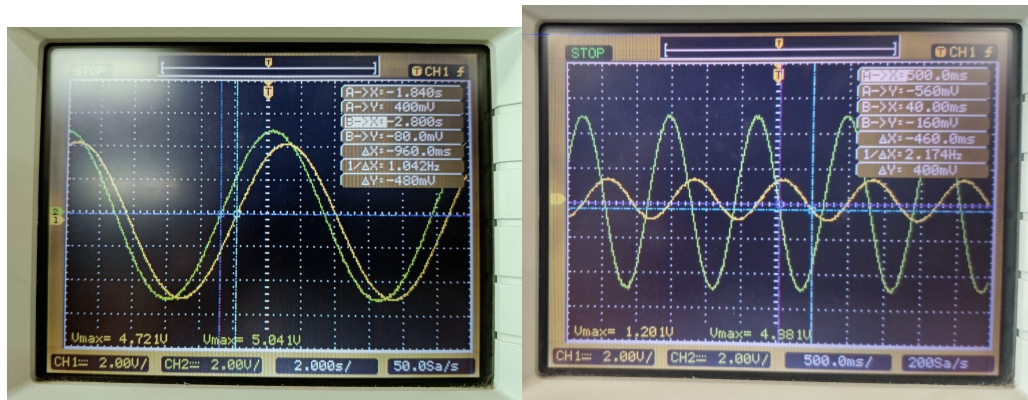

((a)) Caption 1


((b)) Caption 2

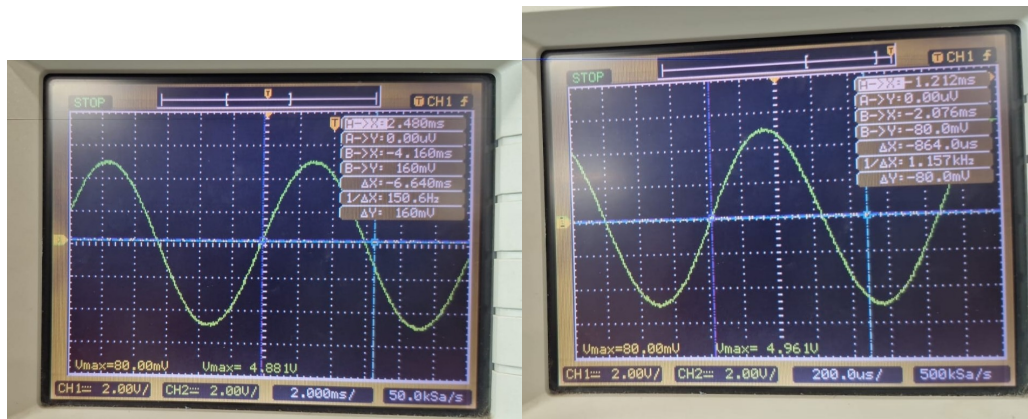

((c)) Caption 3

((d)) Caption 4

Fig. 10: Stage-3

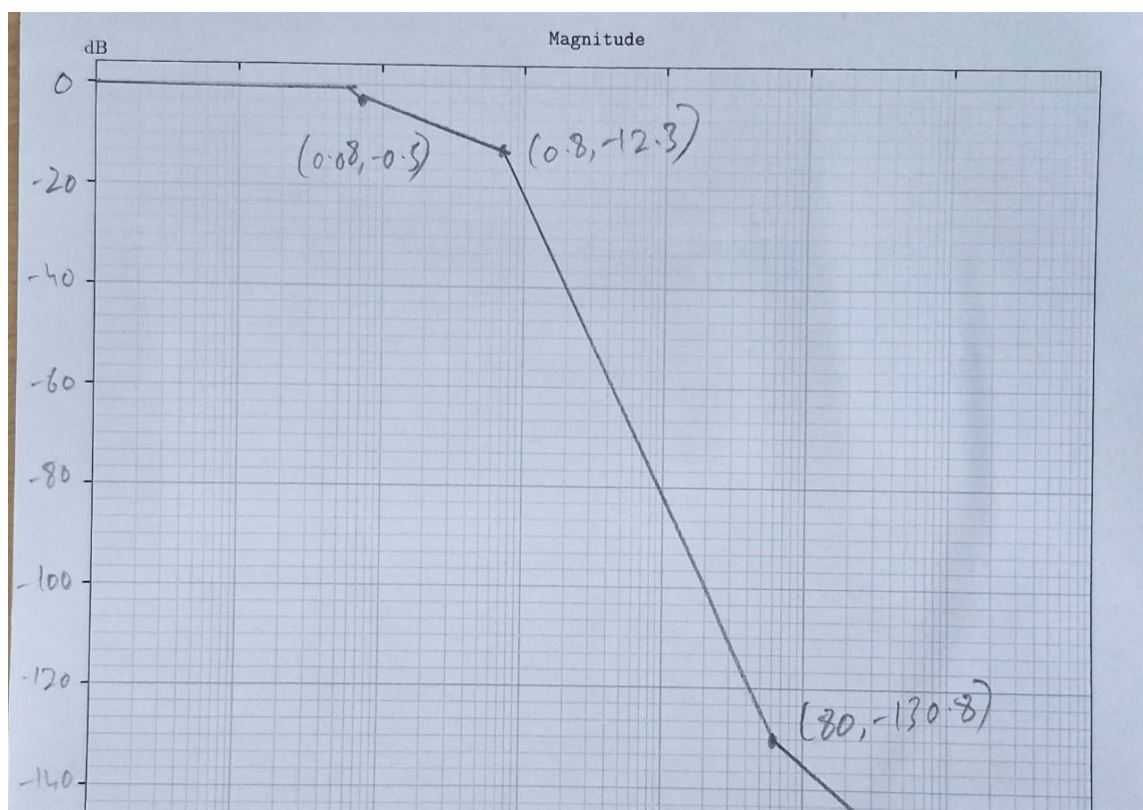



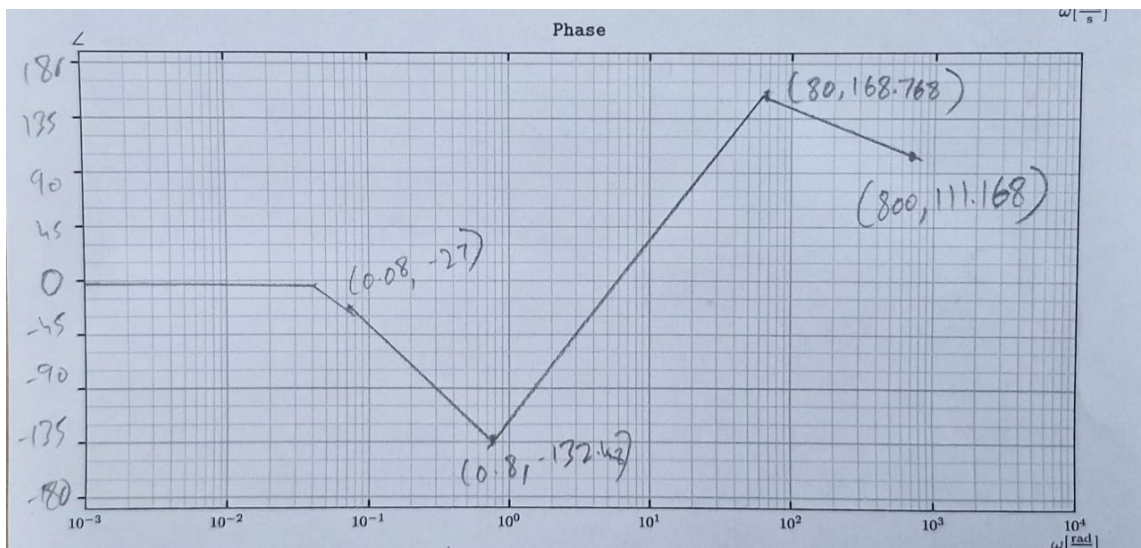


Fig. 12: stage-3 phase